

Intro to Processor Architecture

Y86-64 Sequential + Pipelined processor design

Project Report

Team Members:

Name: V.S.S.Pradhith

Roll no. : 2021102015


Name: K. Vishnu

Roll no. : 2021102034

Overview:


Our goal is to implement a sequential Y86-64 processor as well as a pipelined Y86-64 processor where the sequential processor is implemented in 6 stages (F, D, E, M, WB, PC) and the pipelined one is implemented in 5 stages (F, D, E, M, WB) only. The basic difference between a sequential implementation and a pipelined implementation is as follows:

Unpipelined

 

- Cannot start new operation until previous one completes

3-Way Pipelined

 

- Up to 3 operations in process simultaneously

where OP1, OP2 and OP3 are three operations which has to be implemented respectively.

This is how we can reduce the delay as well as increase the throughput (defined as no. of instructions sent per second) of the design in pipelined model. But still there can be few problems which can be encountered while pipeline architecture is in use such as data dependencies, data hazards, etc which needs to be handled immediately.

In general, we can modify the sequential hardware implementation into pipelined hardware implementation by making few changes by inserting pipeline registers at the end of every stage and excluding the PC update stage as well.

SEQ and PIPE Hardware:

SEQ (sequential processor) and the PIPE (pipelined processor) hardware implementations are almost same as they almost follow similar stages of implementation in common but there are few additional register pipelines in the PIPE hardware. The hardware for both of these implementations are as follows:

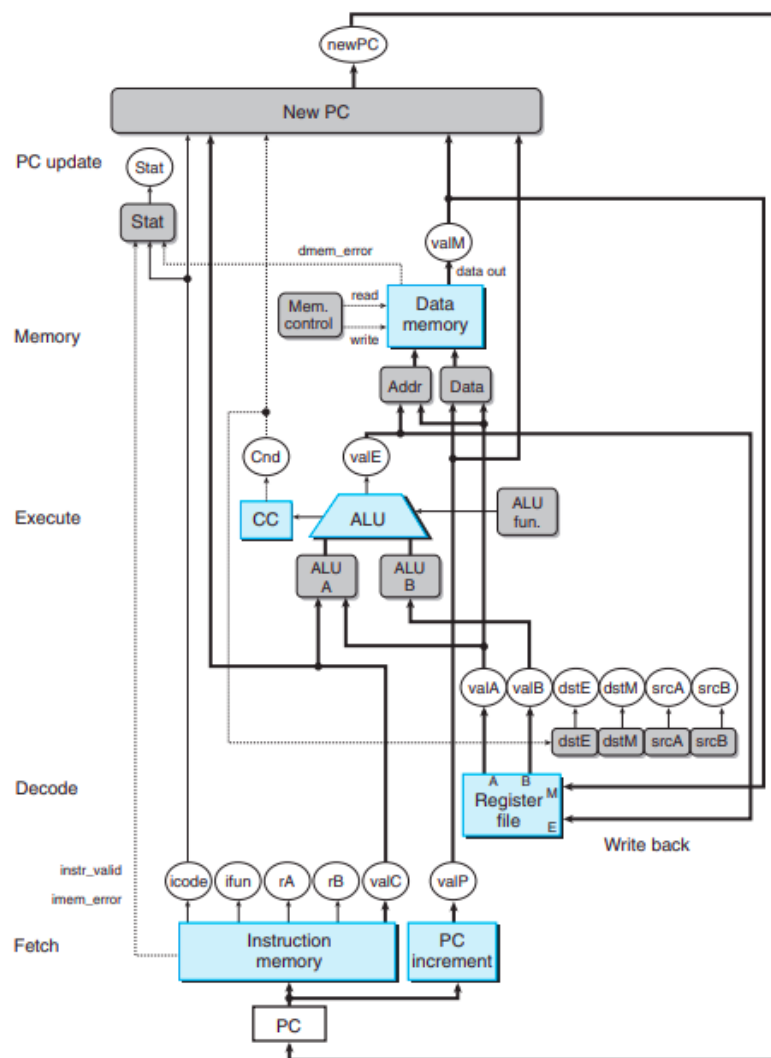


Fig: SEQ hardware implementation

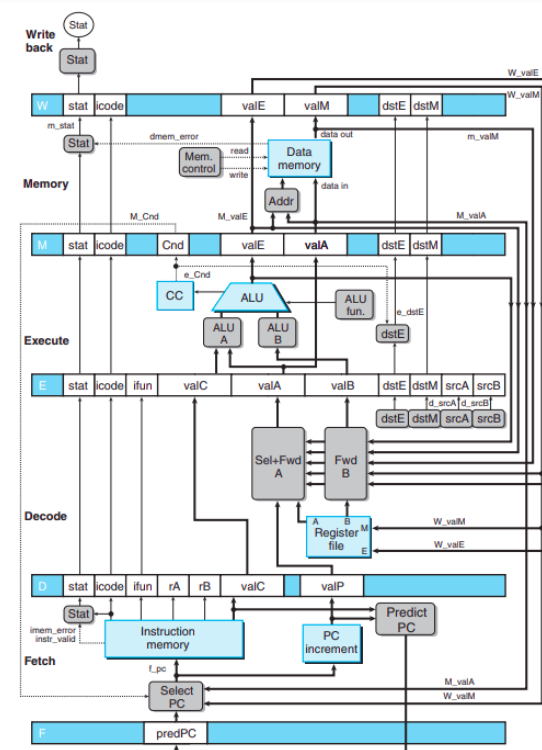


Fig: PIPE hardware implementation

Different instruction stages in SEQ and PIPE processor:

Each instruction goes through following common stages:

- Fetch : Reads instruction from memory
- Decode : Reads program registers
- Execute : Compute value or addresses
- Memory : Read or write data
- Write-back : Write program registers
- PC update (only in SEQ processor) : Updates program counter

Only PC update stage is not available in PIPE design, whereas rest all stages are common in both type of architectures.


The working of above instruction stages for SEQ architecture can be summarised as follows:

Stage	HALT	NOP	CMOV	IRMOVQ
Fch	icode:ifun $\leftarrow M_1[PC]$	icode:ifun $\leftarrow M_1[PC]$	icode:ifun $\leftarrow M_1[PC]$ rA:rB $\leftarrow M_1[PC+1]$	icode:ifun $\leftarrow M_1[PC]$ rA:rB $\leftarrow M_1[PC+1]$ valC $\leftarrow M_8[PC+2]$ valP $\leftarrow PC + 10$
Dec	valP $\leftarrow PC + 1$	valP $\leftarrow PC + 1$	valP $\leftarrow PC + 2$ valA $\leftarrow R[rA]$	
Exe	cpu.stat = HLT		valE $\leftarrow valA$ Cnd $\leftarrow Cond(CC, ifun)$	valE $\leftarrow valC$
Mem				
WB			Cnd ? R[rB] $\leftarrow valE$	R[rB] $\leftarrow valE$
PC	PC $\leftarrow 0$	PC $\leftarrow valP$	PC $\leftarrow valP$	PC $\leftarrow valP$
Stage	RMMOVQ	MRRMOVQ	OPq	jXX
Fch	icode:ifun $\leftarrow M_1[PC]$ rA:rB $\leftarrow M_1[PC+1]$ valC $\leftarrow M_8[PC+2]$ valP $\leftarrow PC + 10$	icode:ifun $\leftarrow M_1[PC]$ rA:rB $\leftarrow M_1[PC+1]$ valC $\leftarrow M_8[PC+2]$ valP $\leftarrow PC + 10$	icode:ifun $\leftarrow M_1[PC]$ rA:rB $\leftarrow M_1[PC+1]$	icode:ifun $\leftarrow M_1[PC]$ valC $\leftarrow M_8[PC+1]$ valP $\leftarrow PC + 9$
Dec	valA $\leftarrow R[rA]$ valB $\leftarrow R[rB]$	valA $\leftarrow R[rA]$ valB $\leftarrow R[rB]$	valA $\leftarrow R[rA]$ valB $\leftarrow R[rB]$	
Exe	valE $\leftarrow valB + valC$	valE $\leftarrow valB + valC$	valE $\leftarrow valB \text{ OP } valA$ Set CC	Cnd $\leftarrow Cond(CC, ifun)$
Mem				
WB	M ₈ [valE] $\leftarrow valA$	valM $\leftarrow M_8[valE]$ R[rA] $\leftarrow valM$	R[rB] $\leftarrow valE$	
PC	PC $\leftarrow valP$	PC $\leftarrow valP$	PC $\leftarrow valP$	PC $\leftarrow Cnd ? valC : valP$
Stage	CALL	RET	PUSHQ	POPQ
Fch	icode:ifun $\leftarrow M_1[PC]$	icode:ifun $\leftarrow M_1[PC]$	icode:ifun $\leftarrow M_1[PC]$ rA:rB $\leftarrow M_1[PC+1]$	icode:ifun $\leftarrow M_1[PC]$ rA:rB $\leftarrow M_1[PC+1]$
Dec	valC $\leftarrow M_8[PC+1]$ valP $\leftarrow PC + 9$	valP $\leftarrow PC + 1$ valA $\leftarrow R[RSP]$	valP $\leftarrow PC + 2$ valA $\leftarrow R[rA]$	valP $\leftarrow PC + 2$ valA $\leftarrow R[RSP]$
Exe	valB $\leftarrow R[RSP]$ valE $\leftarrow valB - 8$	valB $\leftarrow R[RSP]$ valE $\leftarrow valB + 8$	valB $\leftarrow R[RSP]$ valE $\leftarrow valB - 8$	valB $\leftarrow R[RSP]$ valE $\leftarrow valB + 8$
Mem	M ₈ [valE] $\leftarrow valP$	valM $\leftarrow M_8[valA]$	M ₈ [valE] $\leftarrow valA$	valM $\leftarrow M_8[valA]$
WB	R[RSP] $\leftarrow valE$	R[RSP] $\leftarrow valE$	R[RSP] $\leftarrow valE$	R[RSP] $\leftarrow valE$ R[rA] $\leftarrow valM$
PC	PC $\leftarrow valC$	PC $\leftarrow valM$	PC $\leftarrow valP$	PC $\leftarrow valP$

Design logic for each stage in both type of architectures:

a) Fetch stage:


Consider the SEQ fetch stage:

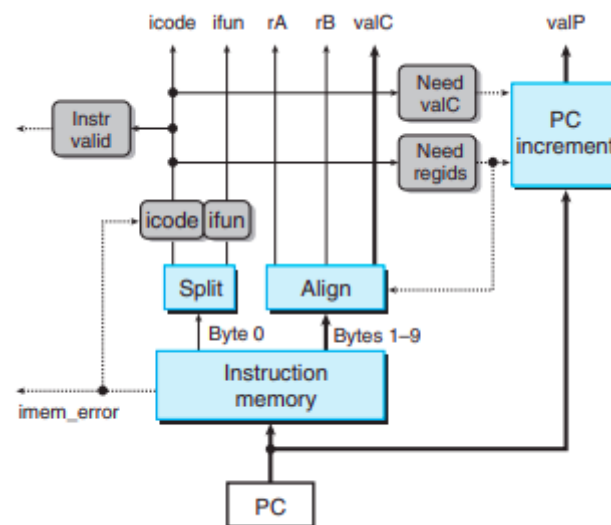

Six bytes are read from the instruction memory using the PC as the starting address. From these bytes, we generate the different instruction fields. The PC increment block computes signal valP.

In fetch stage the processor reads at most 10 bytes of instruction and then it partitions the bytes into 1 byte for **icode** and **ifun** and 1 bytes for registers **rA**, **rB** and remaining 8 bytes as **valC** and sets PC value as **valP**.

Consider the PIPE fetch stage:

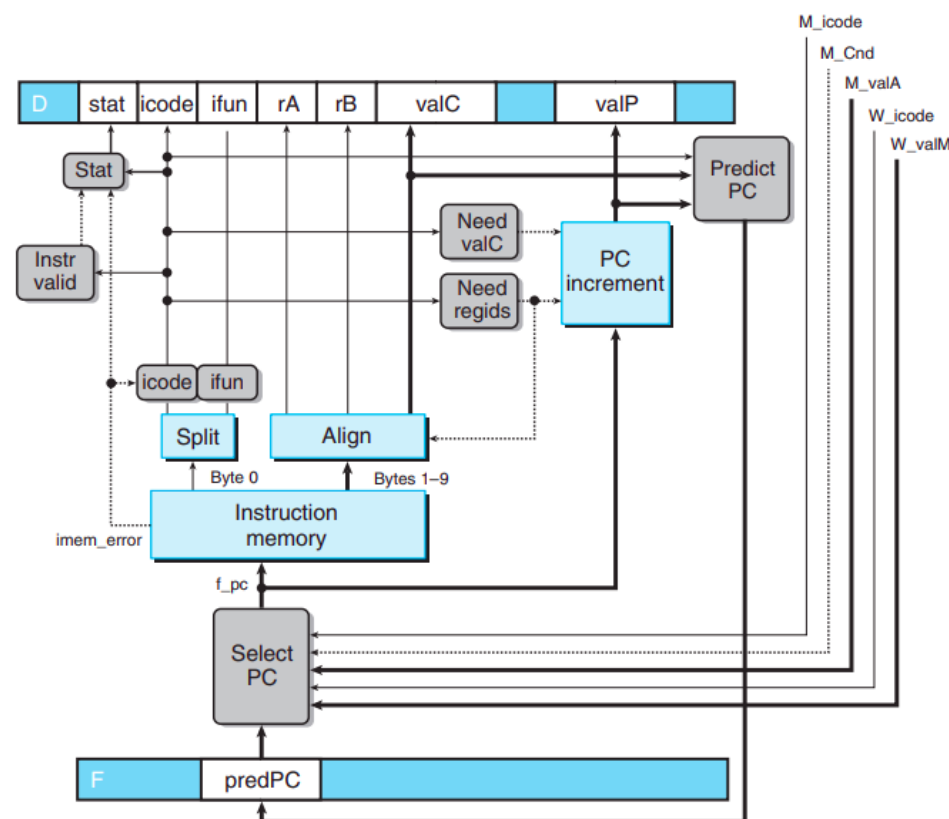

The fundamental building block of PIPE fetch stage is similar to that of the entire SEQ fetch stage. Additionally, there are fetch and decode pipelined registers for storing predicted PC and the signals (valP, valC, rA, rB, etc.) generated in the fetch stage respectively.

As we are not performing PC update stage in PIPE implementation, we are predicting the next PC value and are updating it directly in fetch stage only and this process is called PC prediction.

The value of predicted PC depends on parameters such as **icode**, **valC** and **valP**. Within the one cycle time limit, the processor can only predict the address of the next instruction.

PC prediction strategy :

- i) Instructions that don't transfer control : Predict next PC to valP. This is always reliable.
- ii) Call and unconditional jumps : Predict next PC to be valC (destination). This also always reliable.
- iii) Conditional jumps : Predict next PC to be valC (destination). It's only correct if branch is taken. Typically right 60% of time
- iv) Return instruction : Don't try to predict.

We have referred to the above block diagrams while writing the fetch modules in verilog and the modules are defined as follows:

```
home > vsspradhith > Documents > IPA > Sequential > fetch.v
1  module fetch(clk,icode,ifun,rA,rB,valc,valP,PC,invalid_instr,mem_error,halt,instr);
2      input clk;
3      input [63:0] PC; //this points to the address of instruction;
4      input [0:79]instr; // the maximum length of any instruction is 10bytes = 80bits
5      output reg [3:0] icode,ifun;
6      output reg [63:0] valc; //this is where the displacement or destination value in jump is stores;
7      output reg [3:0] rA,rB; //registers which stores the parameters
8      output reg [63:0] valP; //updated PC value
9      output reg invalid_instr = 0, mem_error = 0; //flages to check memory and second flag is to check valid instruction
10     output reg halt=0;
```

SEQ fetch

```

home > vsspradhith > Documents > IPA > PIPE_LINE > fetch.v
1 module fetch(clk,D_icode,D_ifun,D_rA,D_rB,D_valc,D_valP,f_predPC,M_icode,M_cnd,M_valA,W_icode,W_valM,F_predPC,F_stall,D_stall,D_bubble);
2 //in fetch we can't have bubble but we can have a stall
3 //we need to check the status codes in fetch and pass it to decode
4
5
6 output reg [3:0]D_icode,D_ifun,D_rA,D_rB;
7 output reg [0:3]D_stat = 4'b1000;
8 output reg signed[63:0] D_valc; //displacement or immediate value
9 output reg[63:0] D_valP, f_predPC; //predicted PC from fetch stage
10
11 input clk, M_cnd; //M_cnd used for jmp
12 input [3:0] M_icode, W_icode; //check whether we got jmp||ret in previous instruction
13 input [63:0] M_valA, W_valM; //used when jmp call and return are used
14 input [63:0] F_predPC; //predicted PC
15 input F_stall,D_stall,D_bubble;
16
17 reg [3:0] icode,ifun,rA,rB;
18 reg [63:0]valc,valP,PC;
19 reg mem_error = 0,invalid_instr = 0;
20 reg [0:3]stat_code;
21 reg [0:79] instr;
22 reg [7:0] instr_memory[0:255]; //memory that contains all the instructions


```

PIPE fetch

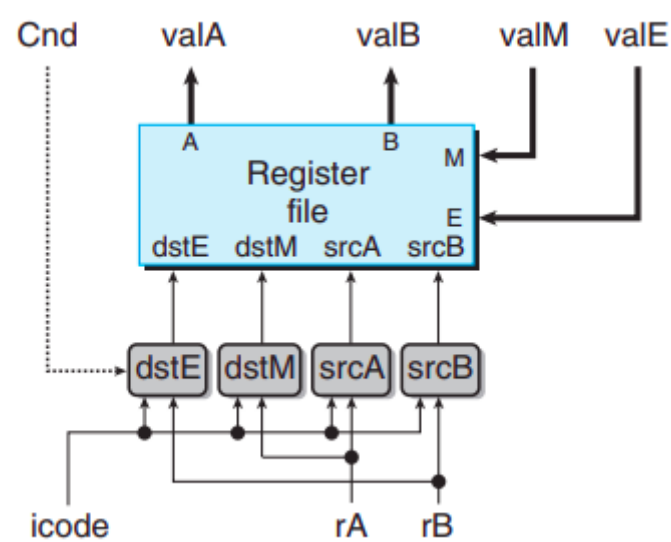b) Decode + Write-back stage:


In both SEQ and PIPE implementations, we are implementing decode and write-back stages collectively as we are dealing with register files which contain registers for reading (decode stage) and writing (write-back stage) the data.

Consider the SEQ decode + write-back stage:



The instruction fields are decoded to generate register identifiers for four addresses (two read and two write) used by the register file. The values read from the register file become the signals valA and valB. The two write-back values valE and valM serve as the data for the writes.

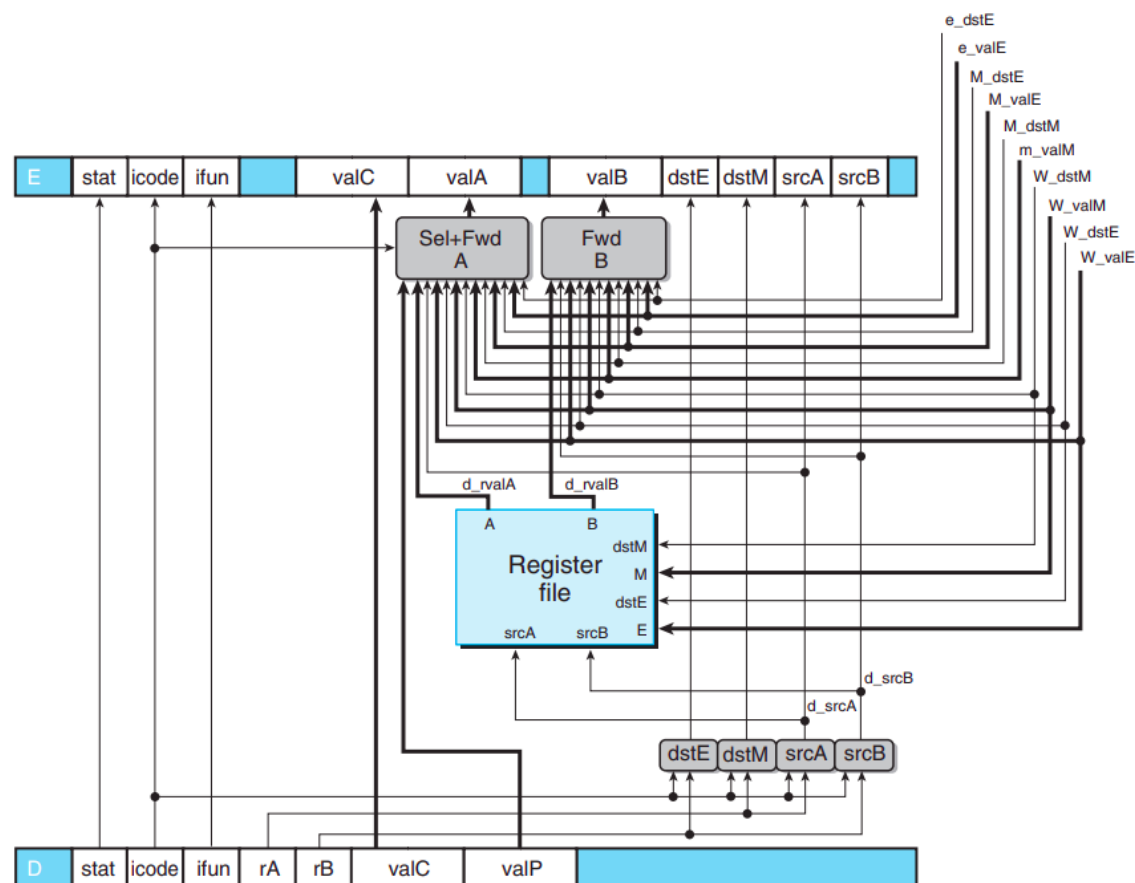Now, consider the PIPE decode + write-back stage:



The fundamental building block of PIPE decode + write-back stage is similar to that of the entire SEQ decode + write-back stage. Additionally, there are decode and execute pipelined registers for storing the signals (**D_valP**, **D_valC**, **rA**, **rB**, etc.) generated in the fetch stage and storing the signals (**E_valP**, **E_valC**, **E_dstM**, **E_dstE**, **E_srcA**, **E_srcB**, etc.) generated in the decode + write-back stage respectively.

No instruction requires both valP and the value read from register port A, and so these two can be merged to form the signal valA for later stages. The block labeled “**Sel+Fwd A**” performs this task and also implements the forwarding logic for source operand valA. The block labeled “**Fwd B**” implements the forwarding logic for source operand valB.

The register write locations are specified by the **dstE** and **dstM** signals from the write-back stage rather than from the decode stage, since it is writing the results of the instruction currently in the write-back stage.

We have referred to the above block diagrams while writing the decode+write-back modules in verilog and we defined our modules as follows:

```

home > vsspradhith > Documents > IPA > Sequential > decode+wb.v
1 //decode and write_back
2 //i wrote both the modules at the same time bacause assigning a register directly with a value and passing it to decode is not happeing in decode so if we give registers
3 //as output and assign values to them in decode it self we will get the correct answer
4
5 module decode(clk, icode, rA, rB,
6               reg_f0,reg_f1,reg_f2,reg_f3,reg_f4,reg_f5,reg_f6,reg_f7,reg_f8,reg_f9,reg_f10,reg_f11,reg_f12,reg_f13,reg_f14,
7               valA,valB,cnd,valM,valE);
8
9     input clk,cnd;
10    input [3:0] icode,rA,rB;
11    output reg signed[63:0] reg_f0,reg_f1,reg_f2,reg_f3,reg_f4,reg_f5,reg_f6,reg_f7,reg_f8,reg_f9,reg_f10,reg_f11,reg_f12,reg_f13,reg_f14; //we have 15 registers in y86-64 processor
12    output reg signed[63:0] valA,valB; //value is updated by a 64 bit number from memory and reg data type is used because we will update the values of outputs conditionally
13    reg signed[63:0] temp_memory[0:14];
14    input signed[63:0] valE;
15    input[63:0] valM;

```

SEQ decode+write-back


```


home > vsspradhith > Documents > IPA > PIPE_LINE > decode_and_write_back.v
1 module decode(clk,D_stat,D_icode,D_ifun,D_rA,D_rB,D_valC,D_valP,e_dstE,e_valE,M_dstE,M_valE,M_dstM,m_valM,W_dstM,
2               W_valM,W_dstE,W_valE,W_icode, E_stat,E_icode,E_ifun,E_valC,E_valA,E_valB,E_dstE,E_dstM,E_srcA,E_srcB,
3               d_srcA,d_srcB, E_bubble, //for pipeline control ie to check datade pendency
4               reg_f0,reg_f1,reg_f2,reg_f3,reg_f4,reg_f5,reg_f6,reg_f7,reg_f8,reg_f9,reg_f10,reg_f11,reg_f12,reg_f13,reg_f14,d_valA,d_valB);
5 //input declarations
6 input clk,E_bubble;
7 input [3:0] D_icode,D_ifun,D_rA,D_rB,W_icode,e_dstE,M_dstE,M_dstM,W_dstE,W_dstM;
8 input [0:3]D_stat; //receives from fetch block whether to check if instruction went normal or not
9 input [63:0] e_valE,M_valE,m_valM,W_valM,W_valE,D_valC,D_valP;
10 //output declarations
11 output reg [0:3]E_stat;
12 output reg [3:0] E_icode,E_ifun,E_dstE,E_dstM,E_srcA,E_srcB,d_srcA,d_srcB;
13 output reg[63:0] E_valC,E_valA,E_valB;
14 output reg[63:0]reg_f0,reg_f1,reg_f2,reg_f3,reg_f4,reg_f5,reg_f6,reg_f7,reg_f8,reg_f9,reg_f10,reg_f11,reg_f12,reg_f13,reg_f14;
15
16
17 //locally used variables declarations as reg's
18 reg[63:0] d_rvalA,d_rvalB; //input to the forwarding logic block
19 output reg[63:0] d_valA,d_valB; //output from forward logic block
20 reg signed[63:0] temp_memory[0:14]; //declaration of an array for our 15 registers
21 reg[3:0] d_dstE,d_dstM ;

```

PIPE decode+write-back


c) Execute stage:

Consider the SEQ execute stage:

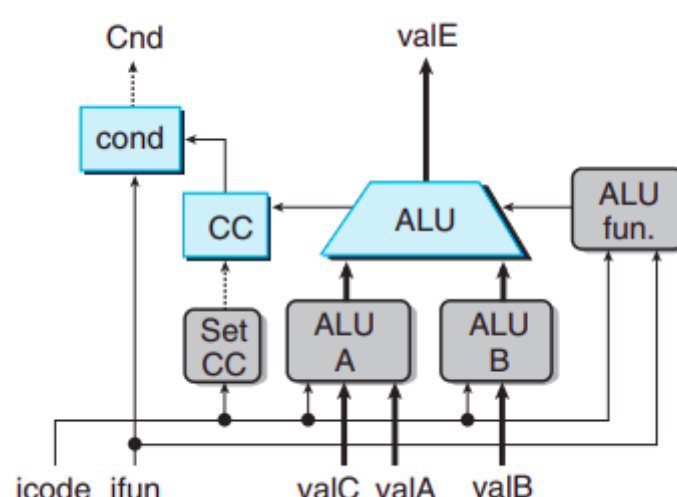

The ALU either performs the operation for an integer operation instruction or acts as an adder. The condition code registers are set according to the ALU value. The condition code values are tested to determine whether a branch should be taken.

Consider the PIPE execute stage:

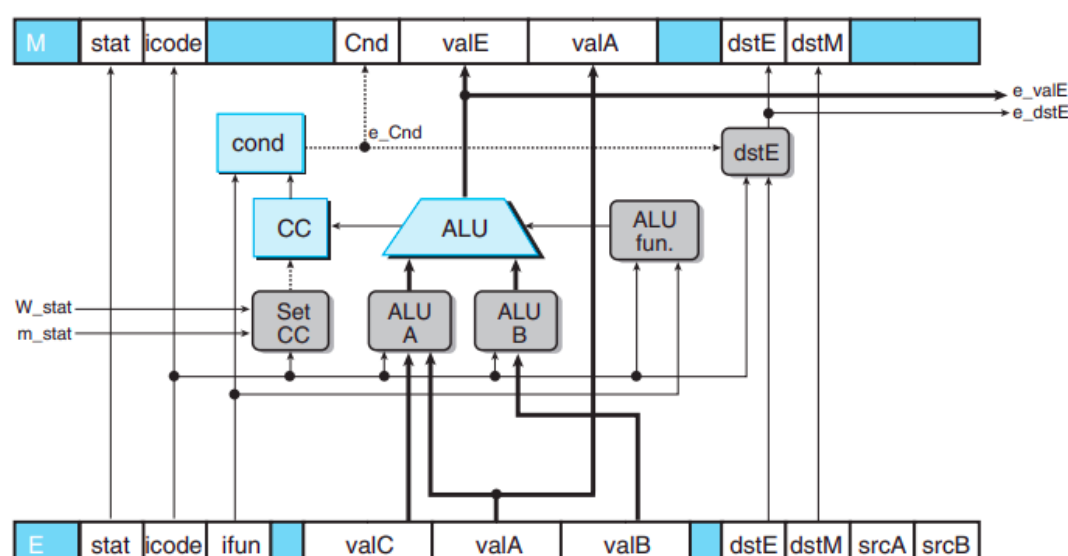

The hardware units and the logic blocks are identical to those in SEQ, with an appropriate renaming of signals. We can see the signals **e_valE** and **e_dstE** directed toward the decode stage as one of the forwarding sources. One difference is that the logic labeled “**Set CC**,” which determines whether or not to update the condition codes, has signals **m_stat** and **W_stat** as inputs.

These signals are used to detect cases where an instruction causing an exception is passing through later pipeline stages, and therefore any updating of the condition codes should be suppressed.

We have referred to the above block diagrams while writing the execute modules in verilog and we defined our modules as follows:

```

home > vsspradhith > Documents > IPA > Sequential > ≡ execute.v
1  `include "../ALU/ALU_module.v"
2  module execute(clk,icode,ifun,vaA,vaB,vaC,vaE,cnd,cc_out,cc_in);
3  //ccin is the input codition codes and used when we execute jump instructions
4  //ccout is the register which stores output flags the order is ZF, SF and OF
5  //vaE stores the final value after operation is done
6  //cnd gives whether the condition is satisfied or not
7  input [3:0] ifun,icode;
8  input clk;
9  input [2:0]cc_in;
10 input signed[63:0] vaA,vaB,vaC;
11 // input [2:0] ccin;
12 output reg cnd;
13 output reg [63:0] vaE;
14 output reg [2:0] cc_out;
15 reg [1:0]control;
16 wire [63:0] vaE_cm,vaE_op,vaE_A,vaE_id;
17 wire cout,OF,temp_OF;//used for sending to alu
18 //vaE_cm => used for cmovxx
19 //vaE_op => used for op
20 //vaE_A ie vaE_assign used for  irmovq.rmmovq,mrmovq
21 //vaE_inc for incrementation in ret and popq annd decrementation in pushq and call

```

SEQ execute

```


home > vsspradhith > Documents > IPA > PIPE_LINE > ≡ execute.v
1  `include "../ALU/ALU_module.v"
2  module execute(clk,E_stat,E_icode,E_ifun,E_valC,E_vaA,E_vaB,E_dstE,E_dstM,//from execute block
3  |           |           |           |           |           |           |           |           |
4  |           |           |           |           |           |           |           |           |
5  |           |           |           |           |           |           |           |           |
6  |           |           |           |           |           |           |           |           |
7  |           |           |           |           |           |           |           |           |
8  |           |           |           |           |           |           |           |           |
9  |           |           |           |           |           |           |           |           |
10 |           |           |           |           |           |           |           |           |
11 |           |           |           |           |           |           |           |           |
12 |           |           |           |           |           |           |           |           |
13 |           |           |           |           |           |           |           |           |
14 |           |           |           |           |           |           |           |           |
15 |           |           |           |           |           |           |           |           |
16 |           |           |           |           |           |           |           |           |
17 |           |           |           |           |           |           |           |           |
18 |           |           |           |           |           |           |           |           |
19 |           |           |           |           |           |           |           |           |
20 |           |           |           |           |           |           |           |           |
21 |           |           |           |           |           |           |           |           |
22 |           |           |           |           |           |           |           |           |
23 |           |           |           |           |           |           |           |           |
24 |           |           |           |           |           |           |           |           |
25 |           |           |           |           |           |           |           |           |
26 |           |           |           |           |           |           |           |           |
27 |           |           |           |           |           |           |           |           |
28 |           |           |           |           |           |           |           |           |
29 |           |           |           |           |           |           |           |           |
30 |           |           |           |           |           |           |           |           |
31 |           |           |           |           |           |           |           |           |
32 |           |           |           |           |           |           |           |           |

```

PIPE execute

d) Memory stage:


Consider, SEQ memory stage:

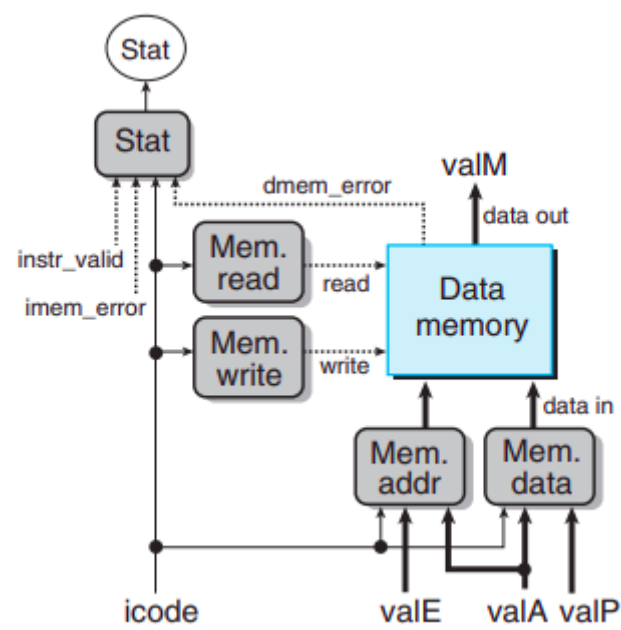

The data memory can either write or read memory values. The value read from memory forms the signal **valM**.

The memory stage has the task of either reading or writing program data. As shown in above figure, two control blocks generate the values for the memory address and the memory input data (for write operations). Two other blocks generate the control signals indicating whether to perform a read or a write operation. When a read operation is performed, the data memory generates the value **valM**.

Consider, PIPE memory stage:

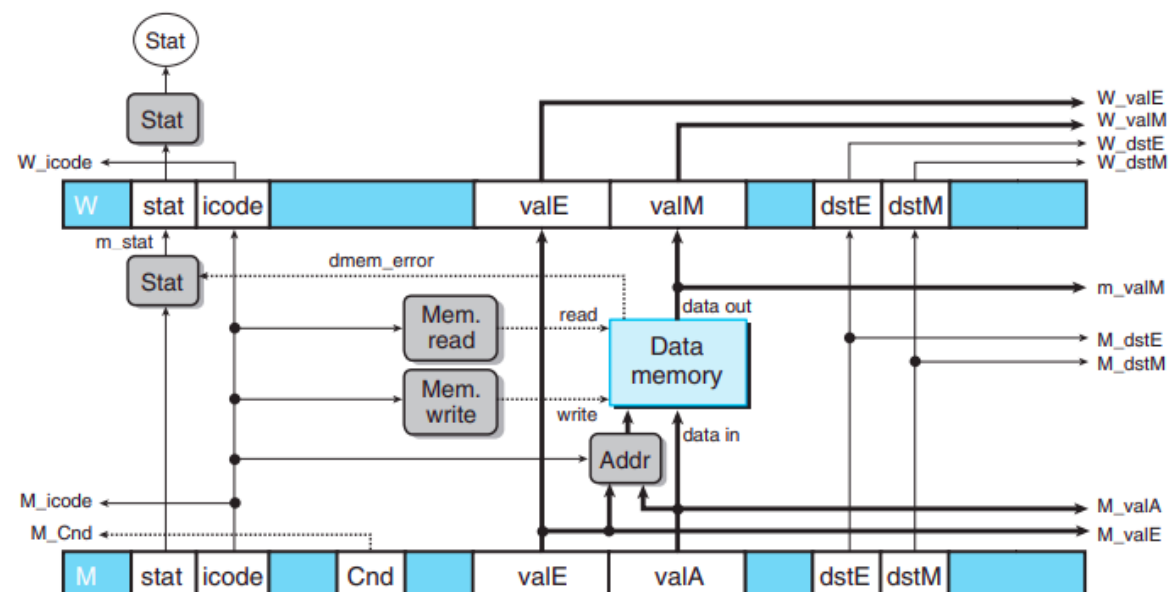

Many of the signals from pipeline registers M and W are passed down to earlier stages to provide write-back results, instruction addresses, and forwarded results.

Comparing this to the memory stage for SEQ, we see that, as noted before, the block labeled "**Mem. data**" in SEQ is not present in PIPE. This block served to select between data sources **valP** (for call instructions) and **valA**, but this selection is now performed by the block labeled "**Sel+Fwd A**" in the decode stage. Most other blocks in this stage are identical to their counterparts in SEQ, with an appropriate renaming of the signals.

In this figure, you can also see that many of the values in pipeline registers M and W are supplied to other parts of the circuit as part of the forwarding and pipeline control logic.

We have referred to the above block diagrams while writing the memory modules in verilog and we defined our modules as follows:

```

home > vsspradhith > Documents > IPA > Sequential > memory.v
1  module memory(clk,icode,valA,valP,valE,valM,m_module_error); //not taking input as valB because we dont use it in memory module
2      input clk;
3      input [3:0]icode;
4      input signed[63:0] valA,valP,valE;
5      output reg[63:0]valM;
6      output reg m_module_error;
7      // output [63:0]m_rsp;
8      reg[63:0] memory[255:0]; //a memory module which has 64bit register files

```

SEQ memory

```

home > vsspradhith > Documents > IPA > PIPE_LINE > memory.v
1  module memory(clk,M_stat,M_icode,M_Cnd,M_valE,M_valA,M_dstE,M_dstM,
2      W_stat,W_icode,W_valE,W_valM,W_dstE,W_dstM,m_valM,m_stat);
3
4      input clk;
5      input [3:0] M_icode;
6      input signed[63:0] M_valA,M_valE;
7      input M_Cnd;
8      input [0:3] M_stat;
9      input [3:0] M_dstE,M_dstM;
10
11     output reg[63:0] W_valM,W_valE,m_valM;
12     output reg [3:0] W_icode,W_dstE,W_dstM;
13     output reg [0:3] W_stat,m_stat;
14
15
16     reg m_module_error = 0;
17     reg[63:0] memory[255:0]; //a memory module which has 64bit register files
18


```

PIPE memory

e) PC update stage:

This stage is only present in SEQ implementation because in PIPE implementation, we are predicting PC in the fetch stage and thus reducing the delay.

Consider the SEQ PC update stage:

 

The next value of the PC is selected from among the signals **valC**, **valM**, and **valP**, depending on the instruction code and the branch flag. The control logic for PC update is as follows:

```

word new_pc = [
    # Call. Use instruction constant
    icode == ICALL : valC;
    # Taken branch. Use instruction constant
    icode == IJXX && Cnd : valC;
    # Completion of RET instruction. Use value from stack
    icode == IRET : valM;
    # Default: Use incremented PC
    1 : valP;
];

```

We have referred to the above block diagram while writing the PC update modules in verilog and we defined our module as follows:

```

home > vsspradhith > Documents > IPA > Sequential > pc_update.v
1 module pc_update(clk,icode,cnd,valc,valM,valP,PC);
2     input clk,cnd;
3     input [3:0]icode;
4     input [63:0]valc,valM,valP;
5     output reg [63:0]PC;

```

SEQ PC update


Pipeline controlling in PIPE implementation:

As discussed earlier, we may face some problems in the pipeline implementation. That can be data hazards, PC misprediction, data dependencies, processing ret, etc.

These all can be handled by doing pipeline controlling. We should implement some control logic that handles this issue. This logic must handle the following four control cases for which other mechanisms, such as data forwarding and branch prediction, do not suffice:

- **Load/use hazards:** The pipeline must stall for one cycle between an instruction that reads a value from memory and an instruction that uses this value.
- **Processing ret:** The pipeline must stall until the ret instruction reaches the write-back stage.
- **Mispredicted branches:** By the time the branch logic detects that a jump should not have been taken, several instructions at the branch target will have started down the pipeline. These instructions must be cancelled, and fetching should begin at the instruction following the jump instruction.
- **Exceptions:** When an instruction causes an exception, we want to disable the updating of the programmer-visible state by later instructions and halt execution once the excepting instruction reaches the write-back stage.

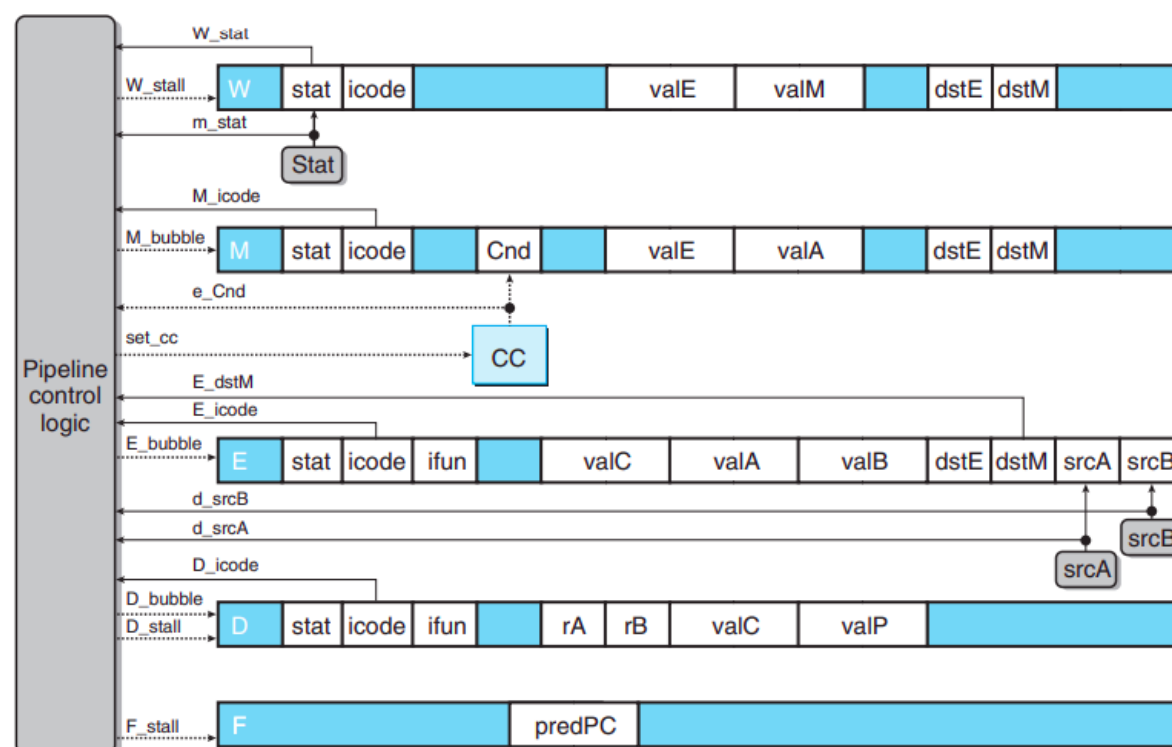Consider the implementation PIPE pipeline control logic:



Based on signals from the pipeline registers and pipeline stages, the control logic generates stall and bubble control signals for the pipeline registers and also determines whether the condition code registers should be updated.

We have referred to the above block diagram while writing the pipeline control logic in verilog and we defined our module as follows:

```

home > vsspradhith > Documents > IPA > PIPE_LINE > ≡ pipeline_control.v
1  module pipeline_control(W_stat,m_stat,M_icode,M_bubble,e_Cnd,setcc,
2      E_dstM,E_icode,E_bubble,d_srcA,d_srcB,D_icode,D_bubble,D_stall,F_stall);
3
4      input [3:0] M_icode,E_dstM,E_icode,d_srcA,d_srcB,D_icode;
5      input e_Cnd;
6      input [0:3] W_stat,m_stat;
7
8      output reg W_stall,M_bubble,setcc,E_bubble,D_bubble,D_stall,F_stall;

```

Pipeline control logic

The control logic for pipe control is as follows:

```

bool F_stall =
    # Conditions for a load/use hazard
    E_icode in { IMRMVQ, IPO PQ } && E_dstM in { d_srcA, d_srcB } ||
    # Stalling at fetch while ret passes through pipeline
    IRET in { D_icode, E_icode, M_icode };

```

```

bool D_stall =
    # Conditions for a load/use hazard
    E_icode in { IMRMVQ, IPO PQ } && E_dstM in { d_srcA, d_srcB };

```

```

bool D_bubble =
    # Mispredicted branch
    (E_icode == IJXX && !e_Cnd) ||
    # Stalling at fetch while ret passes through pipeline
    IRET in { D_icode, E_icode, M_icode }
    # but not condition for a load/use hazard
    && !(E_icode in { IMRMVQ, IPO PQ }
        && E_dstM in { d_srcA, d_srcB });

```

```

bool E_bubble =
    # Mispredicted branch
    (E_icode == IJXX && !e_Cnd) ||
    # Load/use hazard
    E_icode in { IMRMVQ, IPO PQ } && E_dstM in { d_srcA, d_srcB };

```

Testbench for Sequential and Pipelined architecture:

Consider the following set of instructions:

```

instr_memory[1] = 8'h10; //nop
instr_memory[2] = 8'h20; //rrmovq
instr_memory[3] = 8'h12;

```

```

instr_memory[4] = 8'h30;//irmovq
instr_memory[5] = 8'hF2;
instr_memory[6] = 8'h00;
instr_memory[7] = 8'h00;
instr_memory[8] = 8'h00;
instr_memory[9] = 8'h00;
instr_memory[10] = 8'h00;
instr_memory[11] = 8'h00;
instr_memory[12] = 8'h00;
instr_memory[13] = 8'b00000010;

instr_memory[14] = 8'h40;//rmmovq
instr_memory[15] = 8'h24;
{instr_memory[16],instr_memory[17],instr_memory[18],instr_memory[19],instr_memory[20],instr_memory[21],instr_memory[22],instr_memory[23]} = 64'd1;

instr_memory[24] = 8'h40;//rmmovq
instr_memory[25] = 8'h53;
{instr_memory[26],instr_memory[27],instr_memory[28],instr_memory[29],instr_memory[30],instr_memory[31],instr_memory[32],instr_memory[33]} = 64'd0;

instr_memory[34] = 8'h50;//mrmovq
instr_memory[35] = 8'h53;
{instr_memory[36],instr_memory[37],instr_memory[38],instr_memory[39],instr_memory[40],instr_memory[41],instr_memory[42],instr_memory[43]} = 64'd0;

instr_memory[44] = 8'h60;
instr_memory[45] = 8'h9A;

instr_memory[46] = 8'h73;
{instr_memory[47],instr_memory[48],instr_memory[49],instr_memory[50],instr_memory[51],instr_memory[52],instr_memory[53],instr_memory[54]} = 64'd56;

instr_memory[55] = 8'h00;

instr_memory[56] = 8'hA0;
instr_memory[57] = 8'h9F;

instr_memory[58] = 8'hB0;
instr_memory[59] = 8'h9F;

instr_memory[60] = 8'h80;
{instr_memory[61],instr_memory[62],instr_memory[63],instr_memory[64],instr_memory[65],instr_memory[66],instr_memory[67],instr_memory[68]} = 64'd80;

instr_memory[69] = 8'h60;
instr_memory[70] = 8'h56;

instr_memory[71] = 8'h70;
{instr_memory[72],instr_memory[73],instr_memory[74],instr_memory[75],instr_memory[76],instr_memory[77],instr_memory[78],instr_memory[79]} = 64'd46;

instr_memory[80] = 8'h30;//irmovq
instr_memory[81] = 8'hF2;
instr_memory[82] = 8'h00;
instr_memory[83] = 8'h00;
instr_memory[84] = 8'h00;
instr_memory[85] = 8'h00;
instr_memory[86] = 8'h00;
instr_memory[87] = 8'h00;
instr_memory[88] = 8'h00;
instr_memory[89] = 8'b00000010;

instr_memory[90] = 8'h60;
instr_memory[91] = 8'h9A;
instr_memory[92] = 8'h10;

instr_memory[93] = 8'h90;

```

For the first instruction we will be implementing a **nop**,

now we will be implementing some basic instructions such as **rmmovq,irmovq,rmmovq,mrmovq** until we reach instruction number **44**.

Now we will set condition codes using the **opq** operation. where we use 2 register values **rA = 9, rB = A**.

we have **valA = -12345** and **valB = 12345**.

we will get **valE = 0** in execute stage and the condition codes gets updated to **CC = 001 ==> OF,SF,ZF**.

now after **opq** operation we will be having our condition codes updated and we wrote a **je** instruction which has **icode = 7 & ifun = 3**. because of condition codes the jump condition gets satisfied. so the next instruction is updated to 56 instead of 55.

now we have **pushq** in **56th** instruction which pushes value into memory stack and the value of stack is at 254(**rsp**). Because of **pushq**, the **rsp** is reduced to **253** and the value from register 9 is pushed to memory. now we will be moving to instruction number **58**.

we have **popq** in **58th** instruction. **rsp** would be updated to **254** again and the value present at memory location **253** is pushed into the register **9**.

call instruction is implemented in **instr_60** and we will be transferred to a **PC** value of **80**. so call is like a function which shifts operation from current instruction **60** to **80** instead of **69**.

so we will be implementing functions at **80** such as **irmovq, opq,nop** and we will be currently lying at **PC** value **93**.

Now **93** is return function which takes last updated value in stack and this value was updated by call. when we call the instruction, the original progress namely **valP** is updated to memory stack and the **rsp** is located to it.

because we have encountered a return instruction we will be updated with a value of **69** as **valM** which is taken from memory.

now we have reached instruction number **69** which contains **opq** and this updates the condition as **CC = 010**.

after **opq** we have out **PC** at out jump instruction and since its an unconditional jump we would be directly jumping to instruction number **46**.

now because of our new condition codes our **je** condition at instruction number **46** is failed and it is moved to **55** which is a halt instruction.

order of execution is as follows;

1 → 2 → 4 → 14 → 24 → 34 → 44 → 46 → 56 → 58 → 60 →

80 → some call instruction → 93 → 69 → 71 → 46 → 55(halt)

Following results are for the testbench of Pipeline processor:

```
VCD info: dumpfile processor.vcd opened for output.
F_stall = 0 D_stall = 0 D_bubble = 0 setcc = 1 cycle =      1 clk=1 F_predPC=      1 f_predPC=      2
d_srcA = x d_srcB = x
e_cnd = x e_valE =      0 E_valA =      x E_valB =      x E_dstM = x E_dstE = x e_dstE = x
OF = 0 SF = 0 ZF = 0
D_icode=xxxx D_ifun=xxxx D_rA=xxxx D_rB=xxxx, valC=      x
W_valM =      x
rsp =      x and m_valM =      x M_valA =      x M_valE =      x
d_valA =      x d_valB =      x

F_stall = 0 D_stall = 0 D_bubble = 0 setcc = 1 cycle =      2 clk=1 F_predPC=      2 f_predPC=      4
d_srcA = 15 d_srcB = 15
e_cnd = x e_valE =      0 E_valA =      x E_valB =      x E_dstM = x E_dstE = x e_dstE = x
OF = 0 SF = 0 ZF = 0
D_icode=0001 D_ifun=0000 D_rA=xxxx D_rB=xxxx, valC=      x
W_valM =      x
rsp =      254 and m_valM =      x M_valA =      x M_valE =      0
d_valA =      x d_valB =      x

F_stall = 0 D_stall = 0 D_bubble = 0 setcc = 1 cycle =      3 clk=1 F_predPC=      4 f_predPC=      14
d_srcA = 1 d_srcB = 15
e_cnd = x e_valE =      0 E_valA =      x E_valB =      x E_dstM = 15 E_dstE = 15 e_dstE = 15
OF = 0 SF = 0 ZF = 0
D_icode=0010 D_ifun=0000 D_rA=0001 D_rB=0010, valC=      x
W_valM =      x
rsp =      254 and m_valM =      x M_valA =      x M_valE =      0
d_valA =      10 d_valB =      0

F_stall = 0 D_stall = 0 D_bubble = 0 setcc = 1 cycle =      4 clk=1 F_predPC=      14 f_predPC=      24
d_srcA = 15 d_srcB = 15
e_cnd = 1 e_valE =      10 E_valA =      10 E_valB =      0 E_dstM = 15 E_dstE = 2 e_dstE = 2
OF = 0 SF = 0 ZF = 0
D_icode=0011 D_ifun=0000 D_rA=1111 D_rB=0010, valC=      2
W_valM =      x
rsp =      254 and m_valM =      x M_valA =      x M_valE =      0
d_valA =      10 d_valB =      0
```

```

hi1 F_stalled
hi3
F_stall = 1 D_stall = 1 D_bubble = 0 setcc = 1 cycle =      5 clk=1 F_predPC=      24 f_predPC=      34
d_srcA = 2 d_srcB = 4
e_cnd = 1 e_valE =      2 E_valA =      10 E_valB =      0 E_dstM = 15 E_dstE = 2 e_dstE = 2
OF = 0 SF = 0 ZF = 0
D_icode=0100 D_ifun=0000 D_rA=0010 D_rB=0100, valC=      1
W_valM =      x
rsp =      254 and m_valM =      x M_valA =      10 M_valE =      10
d_valA =      2 d_valB =      254

```

```

F_stall = 0 D_stall = 0 D_bubble = 0 setcc = 1 cycle =      6 clk=1 F_predPC=      24 f_predPC=      34
d_srcA = 2 d_srcB = 4
e_cnd = 1 e_valE =      255 E_valA =      2 E_valB =      254 E_dstM = 15 E_dstE = 15 e_dstE = 15
OF = 0 SF = 0 ZF = 0
D_icode=0100 D_ifun=0000 D_rA=0010 D_rB=0100, valC=      1
W_valM =      x
rsp =      254 and m_valM =      x M_valA =      10 M_valE =      2
d_valA =      2 d_valB =      254

```

```

F_stall = 0 D_stall = 0 D_bubble = 0 setcc = 1 cycle =      7 clk=1 F_predPC=      34 f_predPC=      44
d_srcA = 5 d_srcB = 3
e_cnd = 1 e_valE =      255 E_valA =      2 E_valB =      254 E_dstM = 15 E_dstE = 15 e_dstE = 15
OF = 0 SF = 0 ZF = 0
D_icode=0100 D_ifun=0000 D_rA=0101 D_rB=0011, valC=      0
W_valM =      x
rsp =      254 and m_valM =      x M_valA =      2 M_valE =      255
d_valA =      50 d_valB =      3

```

```

F_stall = 0 D_stall = 0 D_bubble = 0 setcc = 1 cycle =      8 clk=1 F_predPC=      44 f_predPC=      46
d_srcA = 15 d_srcB = 3
e_cnd = 1 e_valE =      3 E_valA =      50 E_valB =      3 E_dstM = 15 E_dstE = 15 e_dstE = 15
OF = 0 SF = 0 ZF = 0
D_icode=0101 D_ifun=0000 D_rA=0101 D_rB=0011, valC=      0
W_valM =      x
rsp =      254 and m_valM =      x M_valA =      2 M_valE =      255
d_valA =      50 d_valB =      3

```

```

F_stall = 0 D_stall = 0 D_bubble = 0 setcc = 1 cycle =      9 clk=1 F_predPC=      46 f_predPC=      56
d_srcA = 9 d_srcB = 10
e_cnd = 1 e_valE =      3 E_valA =      50 E_valB =      3 E_dstM = 5 E_dstE = 15 e_dstE = 15
OF = 0 SF = 0 ZF = 0
D_icode=0110 D_ifun=0000 D_rA=1001 D_rB=1010, valC=      0
W_valM =      x
rsp =      254 and m_valM =      x M_valA =      50 M_valE =      3
d_valA =      -12345 d_valB =      12345

```

```

F_stall = 0 D_stall = 0 D_bubble = 0 setcc = 1 cycle =     10 clk=1 F_predPC=      56 f_predPC=      58
d_srcA = 15 d_srcB = 15
e_cnd = 1 e_valE =      0 E_valA =      -12345 E_valB =      12345 E_dstM = 15 E_dstE = 10 e_dstE = 10
OF = 0 SF = 0 ZF = 1
D_icode=0111 D_ifun=0011 D_rA=1001 D_rB=1010, valC=      56
W_valM =      x
rsp =      254 and m_valM =      50 M_valA =      50 M_valE =      3
d_valA =      55 d_valB =      12345

```

```

F_stall = 0 D_stall = 0 D_bubble = 0 setcc = 1 cycle =     11 clk=1 F_predPC=      58 f_predPC=      60
d_srcA = 9 d_srcB = 4
e_cnd = 1 e_valE =      0 E_valA =      55 E_valB =      12345 E_dstM = 15 E_dstE = 15 e_dstE = 15
OF = 0 SF = 0 ZF = 1
D_icode=1010 D_ifun=0000 D_rA=1001 D_rB=1111, valC=      56
W_valM =      50
rsp =      254 and m_valM =      50 M_valA =      -12345 M_valE =      0
d_valA =      -12345 d_valB =      254

```

```

F_stall = 0 D_stall = 0 D_bubble = 0 setcc = 1 cycle =     12 clk=1 F_predPC=      60 f_predPC=      80
d_srcA = 4 d_srcB = 4
e_cnd = 1 e_valE =      253 E_valA =      -12345 E_valB =      254 E_dstM = 15 E_dstE = 4 e_dstE = 4
OF = 0 SF = 0 ZF = 1
D_icode=1011 D_ifun=0000 D_rA=1001 D_rB=1111, valC=      56
W_valM =      50
rsp =      254 and m_valM =      50 M_valA =      55 M_valE =      0
d_valA =      253 d_valB =      253

```

```

F_stall = 0 D_stall = 0 D_bubble = 0 setcc = 1 cycle =     13 clk=1 F_predPC=      80 f_predPC=      90
d_srcA = 15 d_srcB = 4
e_cnd = 1 e_valE =      254 E_valA =      253 E_valB =      253 E_dstM = 9 E_dstE = 4 e_dstE = 4
OF = 0 SF = 0 ZF = 1
D_icode=1000 D_ifun=0000 D_rA=1001 D_rB=1111, valC=      80

```

W_valM =	50				
rsp =	254 and m_valM =	50 M_valA =	-12345 M_valE =	253	
d_valA =	69 d_valB =	254			
F_stall = 0 D_stall = 0 D_bubble = 0 setcc = 1 cycle =	14 clk=1 F_predPC=	90 f_predPC=	92		
d_srcA = 15 d_srcB = 15					
e_cnd = 1 e_valE =	253 E_valA =	69 E_valB =	254 E_dstM = 15 E_dstE =	4 e_dstE =	4
OF = 0 SF = 0 ZF = 1					
D_icode=0011 D_ifun=0000 D_rA=1111 D_rB=0010, valC=	2				
W_valM =	50				
rsp =	254 and m_valM =	-12345 M_valA =	253 M_valE =	254	
d_valA =	254 d_valB =	0			
hi1 F_stalled					
hi3					
F_stall = 1 D_stall = 1 D_bubble = 0 setcc = 1 cycle =	15 clk=1 F_predPC=	92 f_predPC=	93		
d_srcA = 9 d_srcB = 10					
e_cnd = 1 e_valE =	2 E_valA =	254 E_valB =	0 E_dstM = 15 E_dstE =	2 e_dstE =	2
OF = 0 SF = 0 ZF = 1					
D_icode=0110 D_ifun=0000 D_rA=1001 D_rB=1010, valC=	2				
W_valM =	-12345				
rsp =	253 and m_valM =	-12345 M_valA =	69 M_valE =	253	
d_valA =	-12345 d_valB =	0			
F_stall = 0 D_stall = 0 D_bubble = 0 setcc = 1 cycle =	16 clk=1 F_predPC=	92 f_predPC=	93		
d_srcA = 9 d_srcB = 10					
e_cnd = 1 e_valE =	-12345 E_valA =	-12345 E_valB =	0 E_dstM = 15 E_dstE =	10 e_dstE =	10
OF = 0 SF = 1 ZF = 0					
D_icode=0110 D_ifun=0000 D_rA=1001 D_rB=1010, valC=	2				
W_valM =	-12345				
rsp =	254 and m_valM =	-12345 M_valA =	254 M_valE =	2	
d_valA =	-12345 d_valB =	-12345			
F_stall = 0 D_stall = 0 D_bubble = 0 setcc = 1 cycle =	17 clk=1 F_predPC=	93 f_predPC=	93		
d_srcA = 15 d_srcB = 15					
e_cnd = 1 e_valE =	-24690 E_valA =	-12345 E_valB =	-12345 E_dstM = 15 E_dstE =	10 e_dstE =	10
OF = 0 SF = 1 ZF = 0					
D_icode=0001 D_ifun=0000 D_rA=1001 D_rB=1010, valC=	2				
W_valM =	-12345				
rsp =	253 and m_valM =	-12345 M_valA =	-12345 M_valE =	-12345	
d_valA =	-12345 d_valB =	0			
hi2					
hi2					
F_stall = 1 D_stall = 0 D_bubble = 1 setcc = 1 cycle =	18 clk=1 F_predPC=	93 f_predPC=	93		
d_srcA = 4 d_srcB = 4					
e_cnd = 1 e_valE =	0 E_valA =	-12345 E_valB =	0 E_dstM = 15 E_dstE =	15 e_dstE =	15
OF = 0 SF = 0 ZF = 0					
D_icode=1001 D_ifun=0000 D_rA=1001 D_rB=1010, valC=	2				
W_valM =	-12345				
rsp =	253 and m_valM =	-12345 M_valA =	-12345 M_valE =	-24690	
d_valA =	253 d_valB =	253			
hi2					
F_stall = 1 D_stall = 0 D_bubble = 1 setcc = 1 cycle =	19 clk=1 F_predPC=	93 f_predPC=	93		
d_srcA = 15 d_srcB = 15					
e_cnd = 1 e_valE =	254 E_valA =	253 E_valB =	253 E_dstM = 15 E_dstE =	4 e_dstE =	4
OF = 0 SF = 0 ZF = 0					
D_icode=0001 D_ifun=0000 D_rA=0000 D_rB=0000, valC=	0				
W_valM =	-12345				
rsp =	253 and m_valM =	-12345 M_valA =	-12345 M_valE =	0	
d_valA =	253 d_valB =	253			
hi2					
F_stall = 1 D_stall = 0 D_bubble = 1 setcc = 1 cycle =	20 clk=1 F_predPC=	93 f_predPC=	93		
d_srcA = 15 d_srcB = 15					
e_cnd = 1 e_valE =	0 E_valA =	253 E_valB =	253 E_dstM = 15 E_dstE =	15 e_dstE =	15
OF = 0 SF = 0 ZF = 0					
D_icode=0001 D_ifun=0000 D_rA=0000 D_rB=0000, valC=	0				
W_valM =	-12345				
rsp =	253 and m_valM =	69 M_valA =	253 M_valE =	254	
d_valA =	253 d_valB =	253			
F_stall = 0 D_stall = 0 D_bubble = 0 setcc = 1 cycle =	21 clk=1 F_predPC=	93 f_predPC=	71		
d_srcA = 15 d_srcB = 15					
e_cnd = 1 e_valE =	0 E_valA =	253 E_valB =	253 E_dstM = 15 E_dstE =	15 e_dstE =	15
OF = 0 SF = 0 ZF = 0					
D_icode=0001 D_ifun=0000 D_rA=0000 D_rB=0000, valC=	0				
W_valM =	69				

rsp =	253	and m_valM =	69	M_valA =	253	M_valE =	0
d_valA =	253	d_valB =	253				
<hr/>							
F_stall = 0	D_stall = 0	D_bubble = 0	setcc = 1	cycle = 22	clk=1	F_predPC=	71
d_srcA = 5	d_srcB = 6					f_predPC=	46
e_cnd = 1	e_valE =	0	E_valA =	253	E_valB =	253	E_dstM = 15
OF = 0	SF = 0	ZF = 0				E_dstE = 15	e_dstE = 15
D_icode=0110	D_ifun=0000	D_rA=0101	D_rB=0110	valC=	2		
W_valM =	69						
rsp =	254	and m_valM =	69	M_valA =	253	M_valE =	0
d_valA =	50	d_valB =	-143				
<hr/>							
F_stall = 0	D_stall = 0	D_bubble = 0	setcc = 1	cycle = 23	clk=1	F_predPC=	46
d_srcA = 15	d_srcB = 15					f_predPC=	56
e_cnd = 1	e_valE =	-93	E_valA =	50	E_valB =	-143	E_dstM = 15
OF = 0	SF = 1	ZF = 0				E_dstE = 6	e_dstE = 6
D_icode=0111	D_ifun=0000	D_rA=0101	D_rB=0110	valC=	46		
W_valM =	69						
rsp =	254	and m_valM =	69	M_valA =	253	M_valE =	0
d_valA =	80	d_valB =	-143				
<hr/>							
F_stall = 0	D_stall = 0	D_bubble = 0	setcc = 1	cycle = 24	clk=1	F_predPC=	56
d_srcA = 15	d_srcB = 15					f_predPC=	58
e_cnd = 1	e_valE =	0	E_valA =	80	E_valB =	-143	E_dstM = 15
OF = 0	SF = 1	ZF = 0				E_dstE = 15	e_dstE = 15
D_icode=0111	D_ifun=0011	D_rA=0101	D_rB=0110	valC=	56		
W_valM =	69						
rsp =	254	and m_valM =	69	M_valA =	50	M_valE =	-93
d_valA =	55	d_valB =	-143				
<hr/>							
F_stall = 0	D_stall = 0	D_bubble = 0	setcc = 1	cycle = 25	clk=1	F_predPC=	58
d_srcA = 9	d_srcB = 4					f_predPC=	60
e_cnd = 0	e_valE =	0	E_valA =	55	E_valB =	-143	E_dstM = 15
OF = 0	SF = 1	ZF = 0				E_dstE = 15	e_dstE = 15
D_icode=1010	D_ifun=0000	D_rA=1001	D_rB=1111	valC=	56		
W_valM =	69						
rsp =	254	and m_valM =	69	M_valA =	80	M_valE =	0
d_valA =	-12345	d_valB =	254				
<hr/>							
F_stall = 0	D_stall = 0	D_bubble = 0	setcc = 1	cycle = 26	clk=1	F_predPC=	60
d_srcA = 4	d_srcB = 4					f_predPC=	55
e_cnd = 0	e_valE =	253	E_valA =	-12345	E_valB =	254	E_dstM = 15
OF = 0	SF = 1	ZF = 0				E_dstE = 4	e_dstE = 4
D_icode=1011	D_ifun=0000	D_rA=1001	D_rB=1111	valC=	56		
W_valM =	69						
rsp =	254	and m_valM =	69	M_valA =	55	M_valE =	0
d_valA =	253	d_valB =	253				
<hr/>							
halt encountered							

Similarly, following results are for the testbench of sequential processor:

VCD info: dumpfile decode_tb.vcd opened for output.							
1)rsp =	x	PC =	1	clk=1			
2)icode=1	ifun=0	rA= x	rB= x	valC=	x	valP=	2,
3)valA =	0	and valB =	0				
valE =	0	valM =	x				
ccodes OF,SF,ZF cc_in = 000 cc_out=000 and cnd = x							
1)rsp =	254	PC =	2	clk=1			
2)icode=2	ifun=0	rA= 1	rB= 2	valC=	x	valP=	4,
3)valA =	10	and valB =	0				
valE =	10	valM =	x				
ccodes OF,SF,ZF cc_in = 000 cc_out=000 and cnd = 1							
1)rsp =	254	PC =	4	clk=1			

```

2)icode=3 ifun=0 rA=15 rB= 2, valC=          2, valP=          14,

3)valA =          0 and valB =          0
valE =          2 valM =          x
ccodes 0F,SF,ZF cc_in = 000 || cc_out=000 and cnd = 1

1)rsp =          254, PC =          14 clk=1

2)icode=4 ifun=0 rA= 2 rB= 4, valC=          1, valP=          24,

3)valA =          2 and valB =          254
valE =          255 valM =          x
ccodes 0F,SF,ZF cc_in = 000 || cc_out=000 and cnd = 1

1)rsp =          254, PC =          24 clk=1

2)icode=4 ifun=0 rA= 5 rB= 3, valC=          0, valP=          34,

3)valA =          50 and valB =          3
valE =          3 valM =          x
ccodes 0F,SF,ZF cc_in = 000 || cc_out=000 and cnd = 1

1)rsp =          254, PC =          34 clk=1

2)icode=5 ifun=0 rA= 5 rB= 3, valC=          0, valP=          44,

3)valA =          0 and valB =          3
valE =          3 valM =          50
ccodes 0F,SF,ZF cc_in = 000 || cc_out=000 and cnd = 1

1)rsp =          254, PC =          44 clk=1

2)icode=6 ifun=0 rA= 9 rB=10, valC=          0, valP=          46,

3)valA =          -12345 and valB =          12345
valE =          0 valM =          50
ccodes 0F,SF,ZF cc_in = 000 || cc_out=001 and cnd = 1

1)rsp =          254, PC =          46 clk=1

2)icode=7 ifun=3 rA= 9 rB=10, valC=          56, valP=          55,

3)valA =          0 and valB =          0
valE =          0 valM =          50
ccodes 0F,SF,ZF cc_in = 001 || cc_out=010 and cnd = 1

1)rsp =          254, PC =          56 clk=1

2)icode=a ifun=0 rA= 9 rB=15, valC=          56, valP=          58,

3)valA =          -12345 and valB =          254
valE =          253 valM =          50
ccodes 0F,SF,ZF cc_in = 001 || cc_out=010 and cnd = 1

1)rsp =          253, PC =          58 clk=1

2)icode=b ifun=0 rA= 9 rB=15, valC=          56, valP=          60,

3)valA =          253 and valB =          253
valE =          254 valM =          -12345
ccodes 0F,SF,ZF cc_in = 001 || cc_out=010 and cnd = 1

1)rsp =          254, PC =          60 clk=1

2)icode=8 ifun=0 rA= 9 rB=15, valC=          80, valP=          69,

3)valA =          0 and valB =          254
valE =          253 valM =          x
ccodes 0F,SF,ZF cc_in = 001 || cc_out=010 and cnd = 1

1)rsp =          253, PC =          80 clk=1

2)icode=3 ifun=0 rA=15 rB= 2, valC=          2, valP=          90,

3)valA =          0 and valB =          0
valE =          2 valM =          x
ccodes 0F,SF,ZF cc_in = 001 || cc_out=010 and cnd = 1

1)rsp =          253, PC =          90 clk=1

2)icode=6 ifun=0 rA= 9 rB=10, valC=          2, valP=          92,

3)valA =          -12345 and valB =          0
valE =          -12345 valM =          x
ccodes 0F,SF,ZF cc_in = 001 || cc_out=010 and cnd = 1

```



```

1)rsp =                253,PC =                92 clk=1

2)icode=1 ifun=0 rA= 9 rB=10, valc=                2, valP=                93,

3)valA =                0 and valB =                0
valE =                0 valM =                x
ccodes 0F,SF,ZF cc_in = 010 || cc_out=000 and cnd = 1

1)rsp =                253,PC =                93 clk=1

2)icode=9 ifun=0 rA= 9 rB=10, valc=                2, valP=                94,

3)valA =                253 and valB =                253
valE =                254 valM =                69
ccodes 0F,SF,ZF cc_in = 010 || cc_out=000 and cnd = 1

1)rsp =                254,PC =                69 clk=1

2)icode=6 ifun=0 rA= 5 rB= 6, valc=                2, valP=                71,

3)valA =                50 and valB =                -143
valE =                -93 valM =                x
ccodes 0F,SF,ZF cc_in = 010 || cc_out=010 and cnd = 1

1)rsp =                254,PC =                71 clk=1

2)icode=7 ifun=0 rA= 5 rB= 6, valc=                46, valP=                80,

3)valA =                0 and valB =                0
valE =                0 valM =                x
ccodes 0F,SF,ZF cc_in = 010 || cc_out=010 and cnd = 1

1)rsp =                254,PC =                46 clk=1

2)icode=7 ifun=3 rA= 5 rB= 6, valc=                56, valP=                55,


3)valA =                0 and valB =                0
valE =                0 valM =                x
ccodes 0F,SF,ZF cc_in = 010 || cc_out=010 and cnd = 0

halt instruction

```

GTKwave plots:

a) Sequential processor:

 

b) Pipeline processor:

